

## Circuit Basics

### Series Circuits

$$R_T = R_1 + R_2 + \dots + R_n$$

$$V_s = V_1 + V_2 + \dots + V_n$$

$$I_T = I_1 = I_2 = \dots = I_n$$

### Parallel Circuits

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

$$V_s = V_1 = V_2 = \dots = V_n$$

$$I_T = I_1 + I_2 + \dots + I_n$$

## Relativity

$$\gamma = \frac{1}{\sqrt{1 - \frac{v^2}{c^2}}}$$

if  $v = kc$ ,

$$\gamma = \frac{1}{\sqrt{1 - k^2}}$$

$$k = \sqrt{1 - \frac{1}{\gamma^2}}$$

$$t = \gamma t_0$$

$$m = \gamma m_0$$

$$l = \frac{l_0}{\gamma}$$

$$E_{rest} = m_0 c^2$$

$$E_{kinetic} = (\gamma - 1)m_0 c^2$$

$$E_{total} = E_{rest} + E_{kinetic}$$

$$E_{total} = \gamma m_0 c^2$$

## Proper time/length/mass

Measured by an observer at rest relative to the object.


## Michelson Morley Exp.

- Provides experimental evidence that the speed of light is same in all directions (in all inertial reference frames)
- The ether does NOT exist


## Inertial Reference Frames

- Any reference frame that is travelling at a constant velocity.
- All classical laws of physics are obeyed in inertial reference frames.


## Voltage Divider

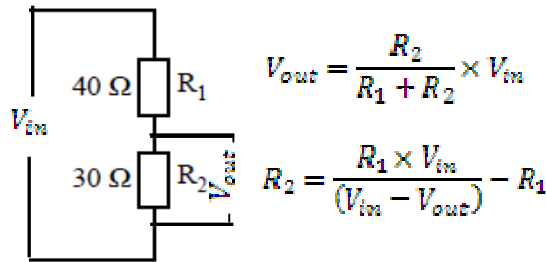

## Amplifiers

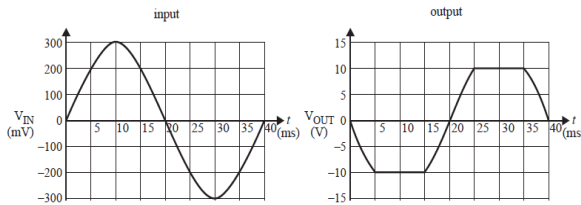


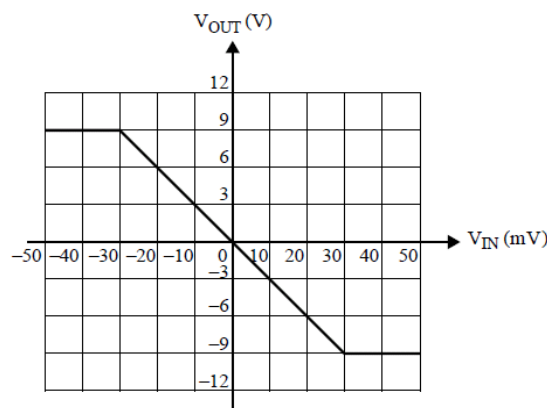**Inverting amplifier:** -signal is flipped



**Inverting amplifier:** negative gradient


## Photodiodes

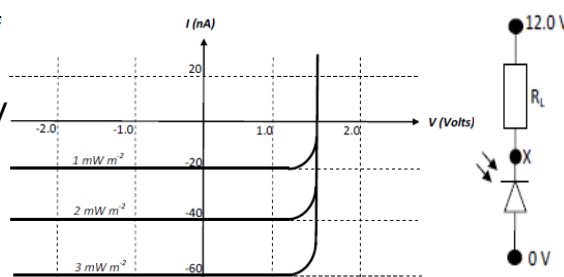

### Photodiodes:


- The current allowed to pass through the diode is dependent on the incident light intensity.
- In reverse bias it is in photoconductive

## Amplitude Modulation

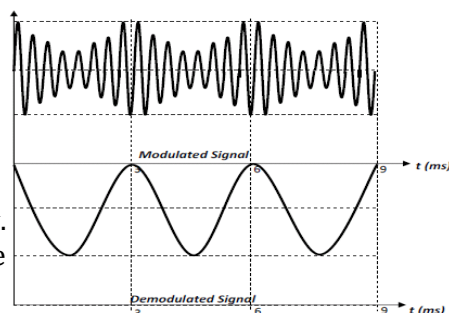

## Thermistors

Resistance depends on temperature

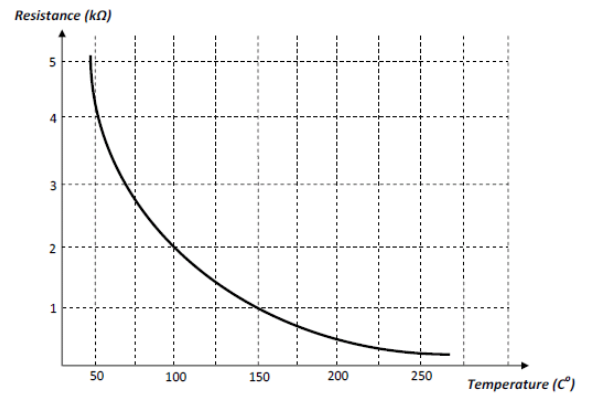


**As the temperature increases:**



- resistance of the thermistor decreases.
- volts across the thermistor decreases.
- the voltage across R1 increases.

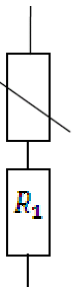**As the temperature decreases:**

- resistance of the thermistor increases.
- volts across the thermistor increases.
- the voltage across R1 decreases.



## Diodes and Light Emitting Diodes

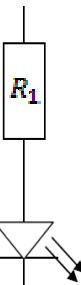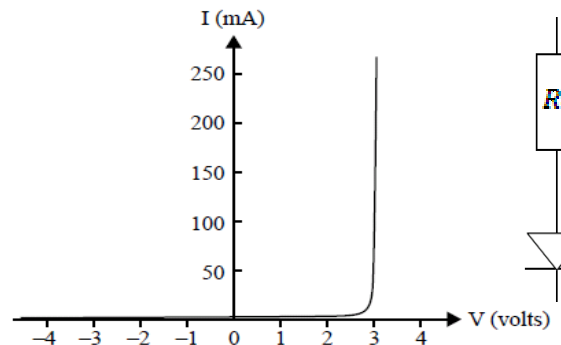


### LED:

Voltage limiting device.

If in forward bias, current can flow through it. Light output increases with greater current.

## Light Dependent Resistors

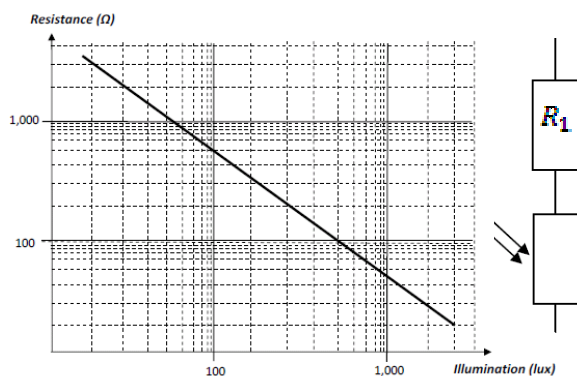

**As the light intensity increases (brighter):**

- resistance of the LDR decreases.
- voltage across the LDR decreases.
- the voltage across R1 increases.

**As the light intensity decreases (darker):**

- resistance of the LDR increases.
- voltage across the LDR increases.
- the voltage across R1 decreases.